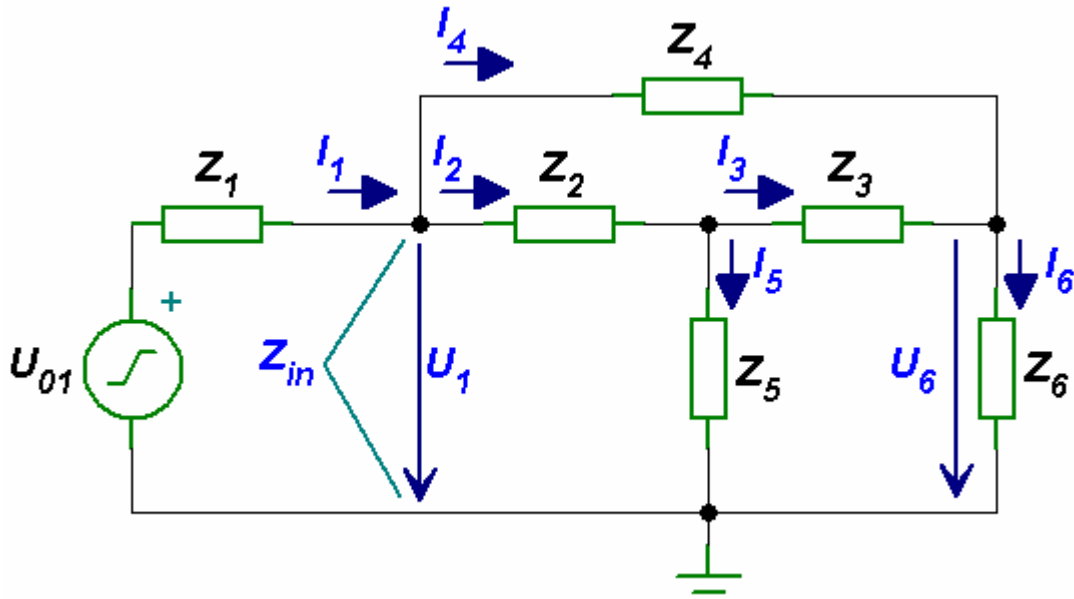


## Nodal Analysis - Incidence Matrix A

### Example


For the circuit shown below find the currents  $I_1$  to  $I_6$ , the voltage  $U_6$ , the input impedance  $Z_{in}$  and the voltage transfer  $K_{06} = U_6 / U_{01}$ . Use incidence matrix  $A$  to solve this task, when  $Z_1 = Z_6 = 50 \Omega$ ,  $Z_2 = Z_3 = -j 50 \Omega$ ,  $Z_4 = Z_5 = j 100 \Omega$ ,  $u_{01}(t) = 10 \cos(\omega t)$  V and  $\omega = 10^5$  rad/s.  $Z_1$  is the internal resistance of the source.



*Circuit with Voltage Source*
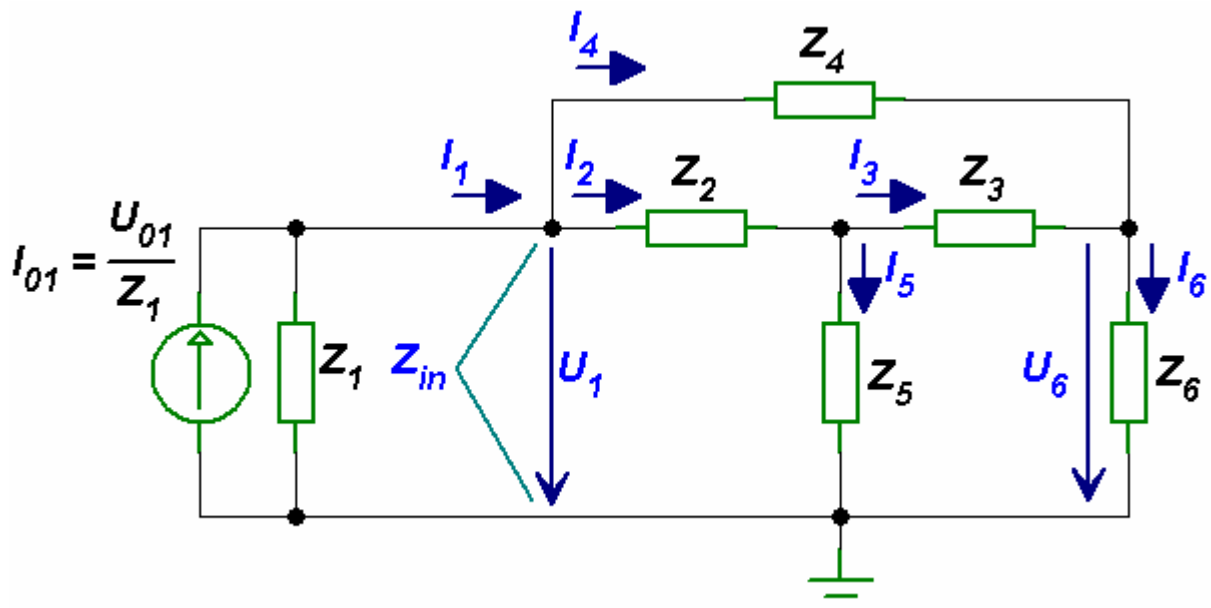
### Solution


After replacing the voltage source by the current source, we obtain the circuit shown below.



*Circuit with Current Source*

For the voltage source given by  $u_{01}(t) = 10 \cos(\omega t)$  the phasor is  $U_{01} = 10 e^{j0^\circ} = 10 \angle 0^\circ$ . The phasor of the current source is
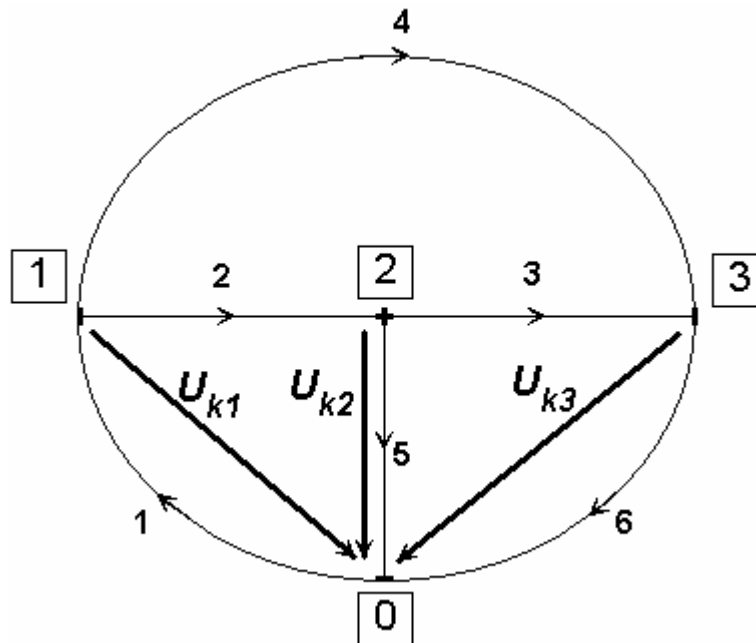
$$I_{01} = \frac{U_{01}}{Z_1} = \frac{10 \angle 0^\circ}{50} = 0.2 \angle 0^\circ \text{ A}$$



*Circuit Diagram*

For the circuit diagram shown above we get the incidence matrix  $\mathbf{A}$ . We assume that the currents leaving a node are positive.

$$\mathbf{A} = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & -1 & -1 & 0 & 1 \end{bmatrix} \begin{matrix} I \\ 2 \\ 3 \end{matrix}$$

The matrix  $\mathbf{I}_0$  of the branch sources and the branch admittance matrix  $\mathbf{Y}$  are

$$\mathbf{I}_0 = \begin{bmatrix} I_{01} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \mathbf{Y} = \begin{bmatrix} 1/Z_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1/Z_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1/Z_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1/Z_4 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1/Z_5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1/Z_6 \end{bmatrix}$$

The matrix of the nodal current sources is

$$\mathbf{I}_{0k} = \mathbf{A} \mathbf{I}_0$$

The nodal admittance matrix is

$$\mathbf{Y}_k = \mathbf{A} \mathbf{Y}^T \mathbf{A} \quad (\mathbf{A}^T \text{ is the transpose of the matrix } \mathbf{A})$$

The nodal voltage matrix is

$$\mathbf{U}_k = -\mathbf{Y}_k^{-1} \mathbf{I}_{0k} \quad (\mathbf{Y}_k^{-1} \text{ is the inverse of the matrix } \mathbf{Y}_k)$$

The branch voltage matrix is

$$\mathbf{U} = \mathbf{A}^T \mathbf{U}_k$$

The input impedance is

$$\mathbf{Z}_{in} = \frac{U_1}{I_1} = \frac{U_{k1}}{I_{01} - \frac{U_{k1}}{Z_1}} \quad (U_{k1} / Z_1 + I_1 = I_{01} \Rightarrow I_1 = I_{01} - U_{k1} / Z_1)$$

The voltage  $U_6$  and the voltage transfer  $K_{06}$  are

$$U_6 = U_{k3} \quad K_{06} = \frac{U_6}{U_{01}} = \frac{U_6}{Z_1 I_{01}}$$

The MATLAB program for solving this task is

### *MATLAB Script*

```
clear; clc
% input values
% the impedances are in ohms
Z1=50; Z2=-j*50; Z3=-j*50; Z4=j*100; Z5=j*100; Z6=50;
% the currents are in amperes
% current i01:
i01max=0.2; i01angle=0; % angle in degrees
% complex representation of the current i01
I01=i01max*exp(j*i01angle*pi/180);
% incidence matrix A
A=[-1  1  0  1  0  0;
    0 -1  1  0  1  0;
    0  0 -1 -1  0  1];
% column matrix I0
I0=[I01; 0; 0; 0; 0; 0];
% diagonal matrix Y
Y=diag([1/Z1 1/Z2 1/Z3 1/Z4 1/Z5 1/Z6]);
I0k=A*I0;
Yk=A*Y*A';
Uk=-inv(Yk)*I0k;
U=A'*Uk
Zin=Uk(1)/(I01-Uk(1)/Z1)
U6=Uk(3)
Ku=U6/(Z1*I01)
```

The results obtained from MATLAB are

```
U =
-9.5000 - 1.5000i
 3.5000 - 0.5000i
 6.5000 + 0.5000i
10.0000 - 0.0000i
 6.0000 + 2.0000i
-0.5000 + 1.5000i

Zin =
5.0000e+001 +3.0000e+002i

U6 =
-0.5000 + 1.5000i

Ku =
-0.0500 + 0.1500i
```