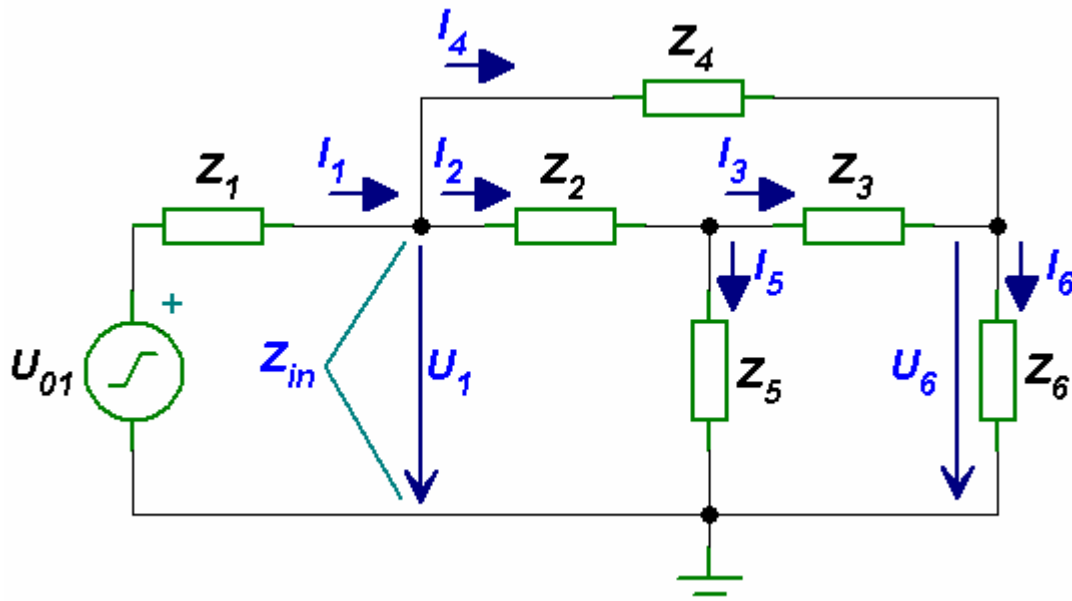


Loop Analysis - Incidence Matrix **B**

Example


For the circuit shown below find the currents I_1 to I_6 , the voltage U_6 , the input impedance Z_{in} and the voltage transfer $K_{06} = U_6 / U_{01}$. Use incidence matrix **B** to solve this task, when $Z_1 = Z_6 = 50 \Omega$, $Z_2 = Z_3 = -j 50 \Omega$, $Z_4 = Z_5 = j 100 \Omega$, $u_{01}(t) = 10 \cos(\omega t)$ V and $\omega = 10^5$ rad/s. Z_1 is the internal resistance of the source.



Circuit

Solution

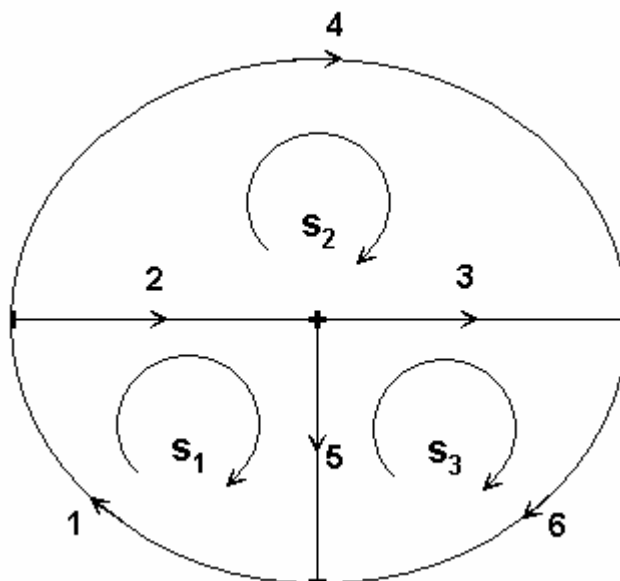For the voltage source given by $u_{01}(t) = 10 \cos(\omega t)$ the phasor is $U_{01} = 10 e^{j0^\circ} = 10 \angle 0^\circ$.



Circuit Diagram

For the circuit diagram shown above we get the incidence matrix \mathbf{B}

$$\mathbf{B} = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 1 & 0 & 0 & 1 & 0 \\ 0 & -1 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & -1 & 1 \end{bmatrix} \begin{matrix} s_1 \\ s_2 \\ s_3 \end{matrix}$$

The matrix \mathbf{U}_0 of the branch sources and the branch impedance matrix \mathbf{Z} are

$$\mathbf{U}_0 = \begin{bmatrix} U_{01} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \mathbf{Z} = \begin{bmatrix} \mathbf{Z}_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & \mathbf{Z}_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & \mathbf{Z}_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & \mathbf{Z}_4 & 0 & 0 \\ 0 & 0 & 0 & 0 & \mathbf{Z}_5 & 0 \\ 0 & 0 & 0 & 0 & 0 & \mathbf{Z}_6 \end{bmatrix}$$

The matrix of the loop voltage sources is

$$\mathbf{U}_{0S} = \mathbf{B} \mathbf{U}_0$$

The loop impedance matrix is

$$\mathbf{Z}_S = \mathbf{B} \mathbf{Z} \mathbf{B}^T \quad (\mathbf{B}^T \text{ is the transpose of the matrix } \mathbf{B})$$

The loop current matrix is

$$\mathbf{I}_S = \mathbf{Z}_S^{-1} \mathbf{U}_{0S} \quad (\mathbf{Z}_S^{-1} \text{ is the inverse of the matrix } \mathbf{Z}_S)$$

The branch current matrix is

$$\mathbf{I} = \mathbf{B}^T \mathbf{I}_S$$

The input impedance is

$$\mathbf{Z}_{in} = \frac{U_1}{I_1} = \frac{U_{01}}{I_1} - \mathbf{Z}_1 \quad (\mathbf{Z}_1 I_1 + U_1 = U_{01} \Rightarrow U_1 = U_{01} - \mathbf{Z}_1 I_1)$$

The voltage U_6 and the voltage transfer \mathbf{K}_{06} are

$$U_6 = \mathbf{Z}_6 I_6 \quad \mathbf{K}_{06} = \frac{U_6}{U_{01}}$$

The MATLAB program for solving this task is

MATLAB Script

```
clear; clc
% input values
% the impedances are in ohms
Z1=50; Z2=-j*50; Z3=-j*50; Z4=j*100; Z5=j*100; Z6=50;
% the voltages are in volts
% voltage u01:
u01max=10; u01angle=0; % angle in degrees
% complex representation of the voltage u01
U01=u01max*exp(j*u01angle*pi/180);
% incidence matrix B
B=[1 1 0 0 1 0;
   0 -1 -1 1 0 0;
   0 0 1 0 -1 1];
% column matrix U0
U0=[U01; 0; 0; 0; 0; 0];
% diagonal matrix Z
Z=diag([Z1 Z2 Z3 Z4 Z5 Z6]);
U0s=B*U0;
Zs=B*Z*B';
Is=inv(Zs)*U0s;
I=B'*Is
Zin=U01/I(1)-Z1
U6=I(6)*Z6
Ku=U6/U01
```

The results obtained from MATLAB are

```
I =
    0.0100 - 0.0300i
    0.0100 + 0.0700i
   -0.0100 + 0.1300i
         0 - 0.1000i
    0.0200 - 0.0600i
   -0.0100 + 0.0300i

Zin =
    5.0000e+001 + 3.0000e+002i

U6 =
   -0.5000 + 1.5000i

Ku =
   -0.0500 + 0.1500i
```