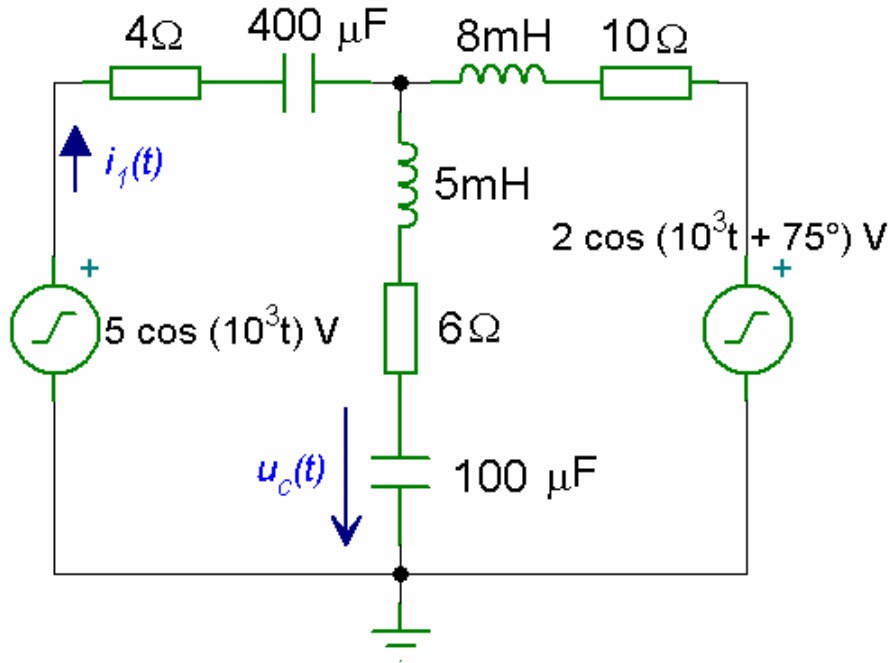


Loop Analysis (AC Analysis)

Example


For the circuit shown below find the current $i_1(t)$ and the voltage $u_c(t)$.



Circuit with Two Sources – Time Domain

Solution

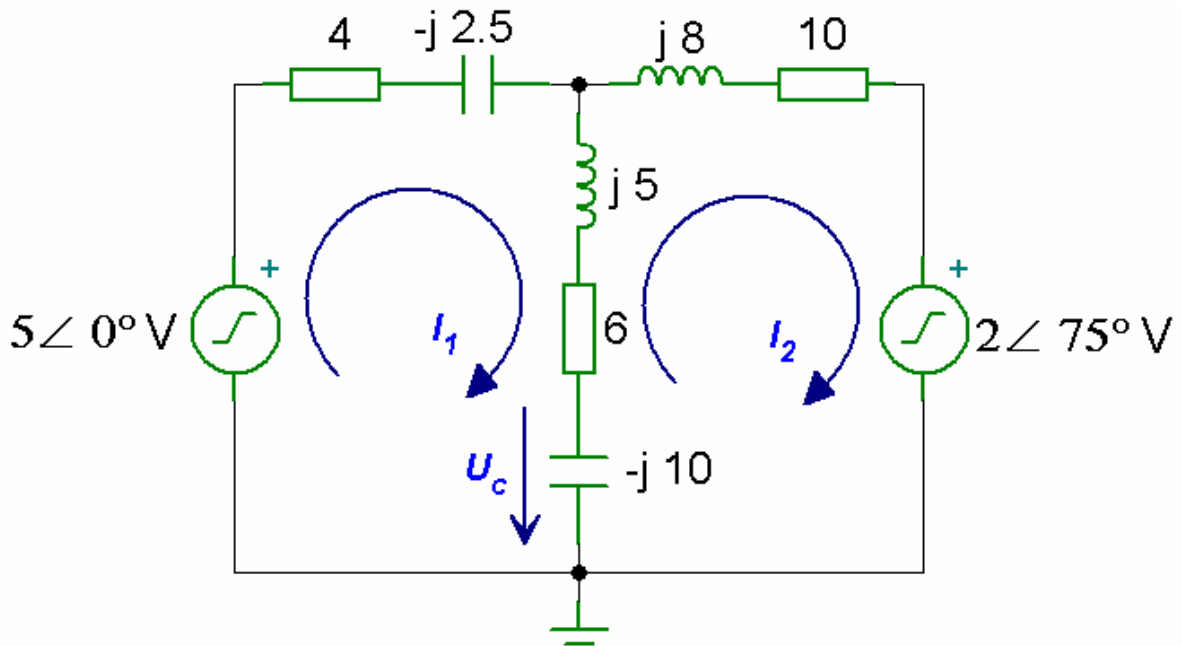Using loop analysis and complex frequency representation we obtain the following figure. The impedances are in ohms.



Circuit with Two Sources – Frequency Domain Equivalent

The loop equations are:

$$\text{Loop 1: } -5\angle 0^\circ + (4 - j 2.5) \mathbf{I}_1 + (6 + j 5 - j 10) (\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$(10 - j 7.5) \mathbf{I}_1 + (-6 + j 5) \mathbf{I}_2 = 5\angle 0^\circ$$

$$\text{Loop 2: } (10 + j 8) \mathbf{I}_2 + 2\angle 75^\circ + (6 + j 5 - j 10) (\mathbf{I}_2 - \mathbf{I}_1) = 0$$

$$(-6 + j 5) \mathbf{I}_1 + (16 + j 3) \mathbf{I}_2 = -2\angle 75^\circ$$

In matrix form, we have

$$\begin{bmatrix} 10 - j 7.5 & -6 + j 5 \\ -6 + j 5 & 16 + j 3 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 5\angle 0^\circ \\ -2\angle 75^\circ \end{bmatrix}$$

The voltage U_C can be obtained as

$$U_C = -j 10 (\mathbf{I}_1 - \mathbf{I}_2)$$

The MATLAB program for solving the loop currents \mathbf{I}_1 , \mathbf{I}_2 and the voltage U_C is

MATLAB Script

```
% This program calculates the phasor current I1 and
% phasor voltage Uc.
% impedance matrix
Z = [10-j*7.5    -6+j*5;
     -6+j*5     16+j*3];
% voltage vector
U = [5; -2*exp(j*75*pi/180)];
I = inv(Z)*U; % solution for loop currents
Uc = -10*j*(I(1)-I(2));
I1_abs = abs(I(1));
I1_ang = angle(I(1))*180/pi;
Uc_abs = abs(Uc);
Uc_ang = angle(Uc)*180/pi;
disp('current I1:')
disp(['magnitude = ', num2str(I1_abs), ' A'])
disp(['angle = ', num2str(I1_ang), ' °'])
disp('_____')
disp('voltage Uc:')
disp(['magnitude = ', num2str(Uc_abs), ' V'])
disp(['angle = ', num2str(Uc_ang), ' °'])
```

The results obtained from MATLAB are

```
current I1:  
magnitude = 0.38771 A  
angle = 15.0193°
```

```
voltage Uc:  
magnitude = 4.2183 V  
angle = -40.8617°
```

From the MATLAB results, the time domain current $i_1(t)$ is

$$i_1(t) = 0.388 \cos(10^3 t + 15.02^\circ) \text{ A}$$

and the time domain voltage $u_C(t)$ is

$$u_C(t) = 4.218 \cos(10^3 t - 40.86^\circ) \text{ V}$$