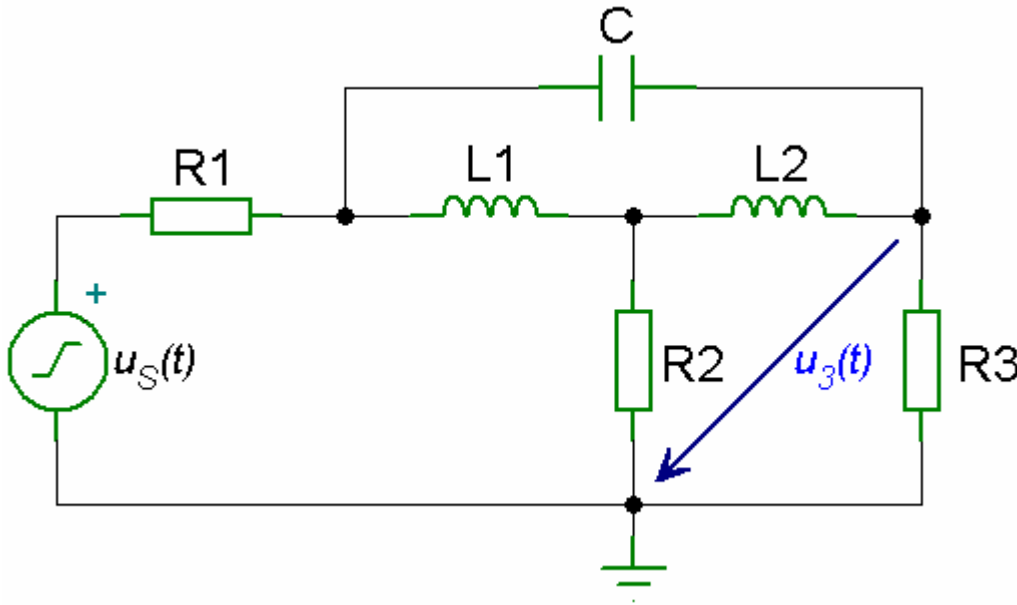


Nodal Analysis (AC Analysis)

Example


For the circuit shown below find the voltage $u_3(t)$ when $R_1 = 20 \Omega$, $R_2 = 100 \Omega$, $R_3 = 50 \Omega$, $L_1 = 4 \text{ H}$, $L_2 = 8 \text{ H}$, $C = 250 \mu\text{F}$, $u_S(t) = 8 \cos(\omega t + 15^\circ) \text{ V}$ and $\omega = 10 \text{ rad/s}$.



RLC Circuit with Sinusoidal Excitation – Time Domain

Solution

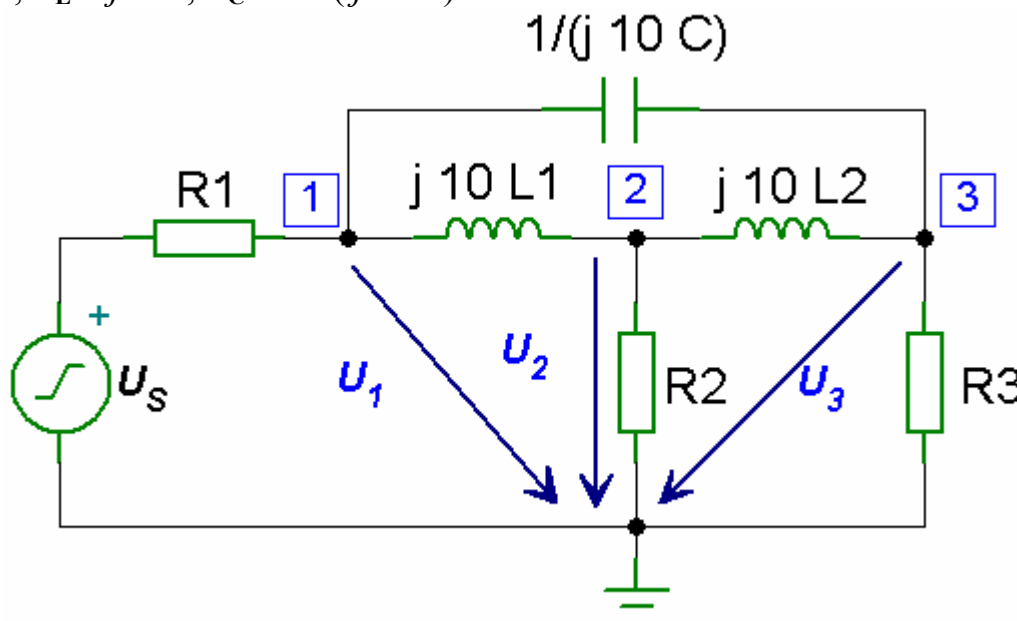Using nodal analysis and complex frequency representation, the analysis can be simplified. For the voltage source given by $u_S(t) = 8 \cos(\omega t + 15^\circ)$ the phasor is $U_S = 8 e^{j15^\circ} = 8 \angle 15^\circ$. For the components R , L , C the complex impedances are $Z_R = R$, $Z_L = j \omega L$, $Z_C = 1 / (j \omega C)$.



RLC Circuit with Sinusoidal Excitation – Frequency Domain Equivalent

Using nodal analysis, we obtain the following equations.

For node 1:

$$-\frac{U_s - U_1}{R_1} + \frac{U_1 - U_2}{j10L_1} + \frac{U_1 - U_3}{\frac{1}{j10C}} = 0$$

$$-\frac{U_s - U_1}{20} - j\frac{U_1 - U_2}{40} + j0.0025(U_1 - U_3) = 0$$

$$0.05 U_1 - j0.025 U_1 + j0.025 U_2 + j0.0025 U_1 - j0.0025 U_3 = 0.05 U_s$$

$$(0.05 - j0.0225) U_1 + j0.025 U_2 - j0.0025 U_3 = 0.4 \angle 15^\circ$$

At node 2:

$$-\frac{U_1 - U_2}{j10L_1} + \frac{U_2}{R_2} + \frac{U_2 - U_3}{j10L_2} = 0$$

$$j\frac{U_1 - U_2}{40} + \frac{U_2}{100} - j\frac{U_2 - U_3}{80} = 0$$

$$j0.025 U_1 - j0.025 U_2 + 0.01 U_2 - j0.0125 U_2 + j0.0125 U_3 = 0$$

$$j0.025 U_1 + (0.01 - j0.0375) U_2 + j0.0125 U_3 = 0$$

At node 3:

$$-\frac{U_1 - U_3}{\frac{1}{j10C}} - \frac{U_2 - U_3}{j10L_2} + \frac{U_3}{R_3} = 0$$

$$-j0.0025(U_1 - U_3) + j\frac{U_2 - U_3}{80} + \frac{U_3}{50} = 0$$

$$-j0.0025 U_1 + j0.0025 U_3 + j0.0125 U_2 - j0.0125 U_3 - 0.02 U_3 = 0$$

$$-j0.0025 U_1 + j0.0125 U_2 + (0.02 - j0.01) U_3 = 0$$

We get the matrix equation

$$\begin{bmatrix} 0.05 - j0.0225 & j0.025 & -j0.0025 \\ j0.025 & 0.01 - j0.0375 & j0.0125 \\ -j0.0025 & j0.0125 & 0.02 - j0.01 \end{bmatrix} \begin{bmatrix} U_1 \\ U_2 \\ U_3 \end{bmatrix} = \begin{bmatrix} 0.4 \angle 15^\circ \\ 0 \\ 0 \end{bmatrix}$$

The MATLAB program for solving voltage U_3 is

MATLAB Script

```
% This program computes the nodal voltage U3
% Y is the admittance matrix
% Us is the voltage source phasor
% I is the current matrix
% U is the voltage vector
Y = [0.05-j*0.0225    j*0.025    -j*0.0025;
     j*0.025        0.01-j*0.0375  j*0.0125;
     -j*0.0025     j*0.0125     0.02-j*0.01];
Us = 8*exp(j*15*pi/180);
I = [0.05*Us; 0; 0];
% solution for nodal voltages
U = inv(Y)*I;
% magnitude of nodal voltage U3
U3_abs = abs(U(3));
% angle of nodal voltage U3 in degrees
U3_ang = angle(U(3))*180/pi;
disp('voltage U3:')
disp(['magnitude = ', num2str(U3_abs), ' V'])
disp(['angle = ', num2str(U3_ang), ' °'])
```

The results obtained from MATLAB are

```
voltage U3:
magnitude = 1.8504 V
angle = -72.4533°
```

From the MATLAB results, the time domain voltage $u_3(t)$ is

$$u_3(t) = 1.85 \cos(\omega t - 72.45^\circ) \text{ V}$$