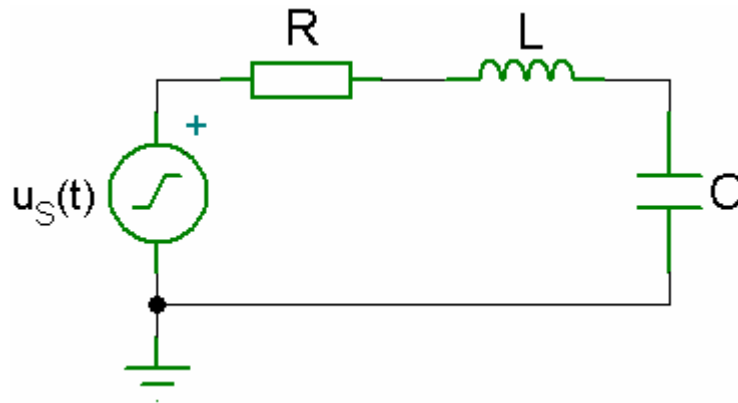


## Phasor Diagram

### Example

For the circuit shown below with using MATLAB plot the phasor diagram and find the complex power  $S$ , the average power  $P$ , the reactive power  $Q$  and the power factor  $\cos \varphi$  when  $R = 5 \Omega$ ,  $L = 20 \text{ mH}$ ,  $C = 400 \mu\text{F}$  and  $u_S(t) = 100 \sin(314t + 20^\circ) \text{ V}$ .



*RLC Circuit*

### Solution

Using complex frequency representation, for the voltage source  $u_S(t)$  the phasor is  $U_S = 100 e^{j 20^\circ} = 100 \angle 20^\circ$ . For the components  $R$ ,  $L$ ,  $C$  the complex impedances are

$$Z_R = R = 5 \Omega$$

$$Z_L = j \omega L = j 314 \cdot 0.020 = j 6.28 = 6.28 \angle 90^\circ \Omega$$

$$\begin{aligned} Z_C &= 1 / (j \omega C) = 1 / (j 314 \cdot 400 \cdot 10^{-6}) = 1 / (j 0.1256) = \\ &= -j 7.9618 = 7.9618 \angle -90^\circ \Omega \end{aligned}$$

The total complex impedance is

$$Z = Z_R + Z_L + Z_C = 5 - j 1.6818 = 5.2753 \angle -18.59^\circ \Omega$$

The current is

$$I = \frac{U_S}{Z} = \frac{100 \angle 20^\circ}{5.275 \angle -18.57^\circ} = 18.9564 \angle 38.59^\circ \text{ A}$$

For the components  $R, L, C$  the voltages are

$$U_R = Z_R I = 94.782 \angle 38.59^\circ \text{ V}$$

$$U_L = Z_L I = 119.0462 \angle 128.59^\circ \text{ V}$$

$$U_C = Z_C I = 150.9268 \angle -51.41^\circ \text{ V}$$

The power factor is

$$\cos \varphi = \cos (\alpha_U - \alpha_I) = \cos (20^\circ - 38.59^\circ) = \cos (-18.59^\circ) = 0.948$$

where  $\alpha_U$  and  $\alpha_I$  are the phase angles of the  $U_S$  and  $I$  phasors

The complex power is

$$\mathbf{S} = U_{\text{RMS}} I_{\text{RMS}}^* = P + jQ \quad [\text{VA}]$$

where  $U_{\text{RMS}}$  and  $I_{\text{RMS}}$  are the phasors of effective values of the voltage  $U_S$  and current  $I$

$$U_{\text{RMS}} = U_{\text{RMS}} \angle \alpha_U = \frac{U_m}{\sqrt{2}} \angle \alpha_U$$

$$I_{\text{RMS}} = I_{\text{RMS}} \angle \alpha_I = \frac{I_m}{\sqrt{2}} \angle \alpha_I$$

and  $I_{\text{RMS}}^*$  is the conjugate of  $I_{\text{RMS}}$

$$I_{\text{RMS}}^* = \frac{I_m}{\sqrt{2}} \angle -\alpha_I$$

Thus

$$\mathbf{S} = \frac{U_m}{\sqrt{2}} \angle \alpha_U \cdot \frac{I_m}{\sqrt{2}} \angle -\alpha_I = 947.82 \angle -18.59^\circ = 898.36 - j302.17 \text{ VA}$$

The average power is the real part of  $\mathbf{S}$   $\Rightarrow P = 898.36 \text{ W}$

The reactive power is the imaginary part of  $\mathbf{S}$   $\Rightarrow Q = -302.17 \text{ VAr}$

Another way to get these powers is

$$P = U_{\text{RMS}} I_{\text{RMS}} \cos(\alpha_U - \alpha_I) = U_{\text{RMS}} I_{\text{RMS}} \cos \varphi$$

$$Q = U_{\text{RMS}} I_{\text{RMS}} \sin(\alpha_U - \alpha_I)$$

where  $U_{\text{RMS}} = \frac{U_m}{\sqrt{2}}$  and  $I_{\text{RMS}} = \frac{I_m}{\sqrt{2}}$

The MATLAB program for solving this task is

### *MATLAB Script*

```
clear; clc;
% this program computes variables of RLC circuit
% and plots the phasor diagram
R = 5; % ohms
L = 20e-3; % H
C = 400e-6; % F
us_max = 100; % V
us_ang = 20; % angle in degrees
w = 314;
% complex representation of the source voltage
Us=us_max*exp(j*us_ang*pi/180);
% complex impedances
ZR=R; ZL=j*w*L; ZC=1/(j*w*C); Z=ZR+ZL+ZC;
% current and voltages
I=Us/Z; UR=ZR*I; UL=ZL*I; UC=ZC*I;
% RMS phasors
U_RMS=Us/sqrt(2); I_RMS=I/sqrt(2);
disp('The complex power is'); S=U_RMS*conj(I_RMS)
disp('The average power is'); P=real(S)
disp('The reactive power is'); Q=imag(S)
disp('The power factor is'); pf=cos(angle(S))
% phasor diagram
line([0 real(UR)], [0 imag(UR)], 'marker', '>');
text(1.05*real(UR), 1.05*imag(UR), 'UR');
line([0 real(UL)], [0 imag(UL)], 'marker', '>');
text(1.05*real(UL), 1.05*imag(UL), 'UL');
line([0 real(UC)], [0 imag(UC)], 'marker', '>');
text(1.05*real(UC), 1.05*imag(UC), 'UC');
line([0 real(Us)], [0 imag(Us)], 'marker', '>');
text(1.05*real(Us), 1.05*imag(Us), 'Us');
line([0 real(I)], [0 imag(I)], 'marker', '+', 'color', 'red');
text(real(I), 2*imag(I), 'I');
axis(1.5*us_max*[-1 1 -1 1]);
xlabel('Re'); ylabel('Im');
grid on; axis square;
```

The results obtained from MATLAB are

```
The complex power is  
S =  
8.9836e+002 -3.0217e+002i  
The average power is  
P =  
898.3630  
The reactive power is  
Q =  
-302.1704  
The power factor is  
pf =  
0.9478
```

The phasor diagram obtained from MATLAB is

