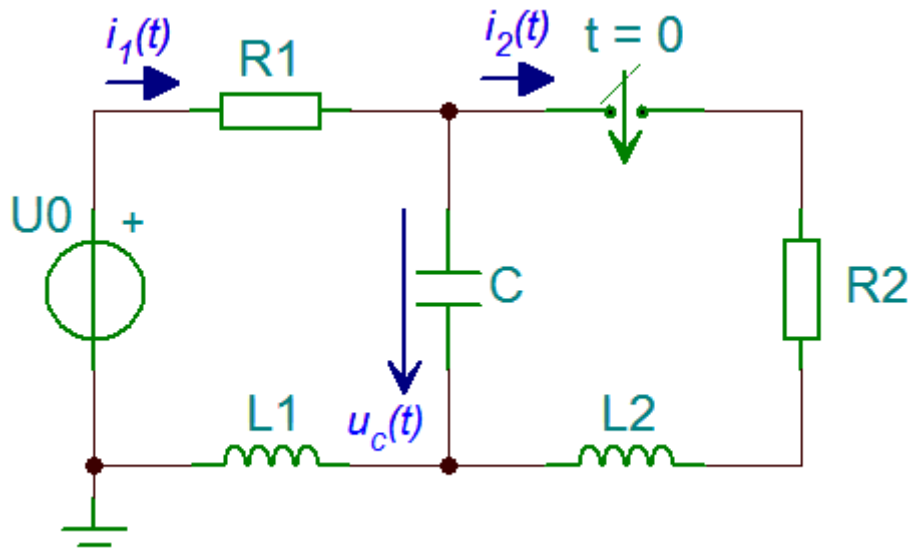


Practicing

Exercise 1 - Transient Analysis

For the circuit shown below find the currents $i_1(t)$, $i_2(t)$ and the voltage $u_C(t)$. Use a numerical solution to the differential equations (graphs for end time = 0.01 s), when $R_1 = 5 \Omega$, $R_2 = 5 \Omega$, $L_1 = 5 \text{ mH}$, $L_2 = 10 \text{ mH}$, $C = 50 \mu\text{F}$ and $U_0 = 20 \text{ V}$. The switch has been opened for a long time.



Circuit

Fill in differential equations in matrix form and values of initial conditions and values of steady states.

$$\begin{bmatrix} \frac{di_1(t)}{dt} \\ \frac{di_2(t)}{dt} \\ \frac{du_C(t)}{dt} \end{bmatrix} = \begin{bmatrix} & & \\ & & \\ & & \end{bmatrix} \cdot \begin{bmatrix} i_1(t) \\ i_2(t) \\ u_C(t) \end{bmatrix} + \begin{bmatrix} \\ \\ \end{bmatrix}$$

$$\begin{bmatrix} i_1(0) \\ i_2(0) \\ u_C(0) \end{bmatrix} = \begin{bmatrix} \\ \\ \end{bmatrix} \qquad \begin{bmatrix} i_1(\infty) \\ i_2(\infty) \\ u_C(\infty) \end{bmatrix} = \begin{bmatrix} \\ \\ \end{bmatrix}$$

Exercise 2 - Nodal Analysis


For the circuit shown below find the branch currents I_1 to I_6 (maximum value and phase degree), the nodal voltages U_1 to U_3 and the active power P supplied by the source. For impedances use a general label Z_i .

Print of the nodal voltages to file "voltages.txt" in the form (example):

$$U_{1m} = 20.00 \angle -60^\circ \text{ [V]}$$

Circuit values are

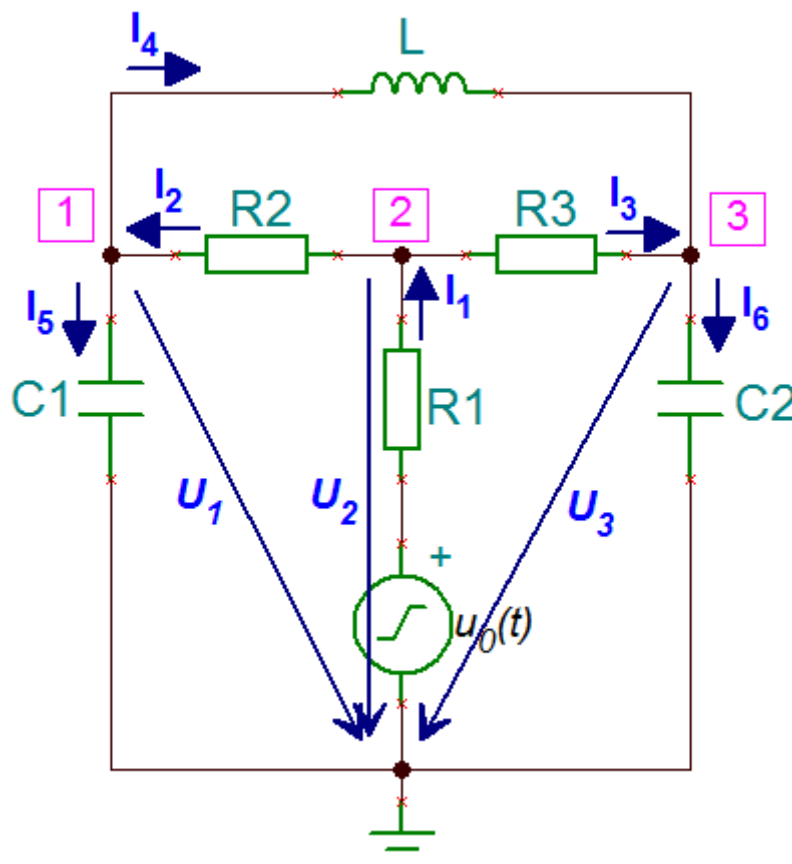$R_1 = 50 \Omega$, $R_2 = 20 \Omega$, $R_3 = 50 \Omega$, $L = 100 \text{ mH}$, $C_1 = 25 \mu\text{F}$, $C_2 = 25 \mu\text{F}$,
 $u_0(t) = 200 \sin(\omega t + 30^\circ) \text{ V}$ and $\omega = 10^3 \text{ rad/s}$.



Circuit